

## Datapath – Vhdl – Part B

Niall Martin Ryan - 14315886

### Datapath.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity DataPath is
port(
    des_sel : in std_logic_vector(2 downto 0);
    load_enable : in std_logic;
    dataS : in std_logic;
    A_sel : in std_logic_vector(2 downto 0);
    B_sel : in std_logic_vector(2 downto 0);
    instruction_MB : in std_logic_vector(15 downto 0);
    INL : in std_logic;
    INR : in std_logic;
    Data_in : in std_logic_vector(15 downto 0);
    Clk : in std_logic;
    fselect : in std_logic_vector(4 downto 0);
    MB_sel : in std_logic;
    MD_sel : in std_logic;
    v : out std_logic;
    c : out std_logic;
    n : out std_logic;
    z : out std_logic;
    Adrs_out : out std_logic_vector(15 downto 0);
    Data_out_bus_b : out std_logic_vector(15 downto 0);
    Control_word : in std_logic_vector(16 downto 0)
);
end DataPath;
architecture Behavioral of DataPath is
    -- signals
    signal reg0_q, reg1_q, reg2_q, reg3_q, reg4_q, reg5_q, reg6_q, reg7_q : std_logic_vector(15 downto 0);
    signal A_output, B_output, Mb_output, Md_output, functional_unit_output : std_logic_vector(15 downto 0);
    signal A_address_out, B_data_out : std_logic_vector(15 downto 0);
    -- control word signal
    signal control_word_transfer : std_logic_vector (16 downto 0);
```

```

component Reg_File port(
d0 : in STD_LOGIC;
    d1 : in STD_LOGIC;
    d2 : in STD_LOGIC;
    m0 : in STD_LOGIC;
    m1 : in STD_LOGIC;
    m2 : in STD_LOGIC;
        m3 : in STD_LOGIC;
        m4 : in STD_LOGIC;
        m5 : in STD_LOGIC;
    data : in STD_LOGIC_VECTOR(15 DOWNTO 0);
    dataS : in STD_LOGIC;
    Clk : in STD_LOGIC;
Data_into_reg : in STD_LOGIC_VECTOR(15 downto 0);
src_output_a : out std_logic_vector(15 downto 0);
src_output_b : out std_logic_vector(15 downto 0);

```

```

    R0 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R1 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R2 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R3 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R4 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R5 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R6 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R7 : out STD_LOGIC_VECTOR(15 DOWNTO 0));

```

```

end component;

```

```

component Mux_2_1 port(
    sel : in std_logic;
    a : in std_logic_vector(15 downto 0);
    b : in std_logic_vector(15 downto 0);
    g : out std_logic_vector(15 downto 0)

```

```

);

```

```

end component;

```

```

component Functional_Unit port(
    fsel : in std_logic_vector(4 downto 0);
    a : in std_logic_vector(15 downto 0);
    b : in std_logic_vector(15 downto 0);
    IL : in std_logic;
    IR : in std_logic;
    f : out std_logic_vector(15 downto 0);
    v : out std_logic;
    c : out std_logic;
    n : out std_logic;

```

```

        z : out std_logic
    );
end component;
begin

```

```

control_word_transfer <= Control_word;
control_word_transfer(16) <= des_sel(2);
control_word_transfer(15) <= des_sel(1);
control_word_transfer(14) <= des_sel(0);
control_word_transfer(13) <= A_sel(2);
control_word_transfer(12) <= A_sel(1);
control_word_transfer(11) <= A_sel(0);
control_word_transfer(10) <= B_sel(2);
control_word_transfer(9) <= B_sel(1);
control_word_transfer(8) <= B_sel(0);
control_word_transfer(7) <= MB_sel;
control_word_transfer(6) <= fselect(4);
control_word_transfer(5) <= fselect(3);
control_word_transfer(4) <= fselect(2);
control_word_transfer(3) <= fselect(1);
control_word_transfer(2) <= fselect(0);
control_word_transfer(1) <= MD_sel;
control_word_transfer(0) <= dataS;

```

```

functional : Functional_Unit port map(
    fsel => fselect,
    a => A_output,
    b => Mb_output,
    f => functional_unit_output,
    IR => INL,
    IL => INR,
    v => v,
    c => c,
    n => n,
    z => z
);

```

```

reg : Reg_File port map(
    d0 => des_sel(0),
    d1 => des_sel(1),
    d2 => des_sel(2),
    m0 => A_sel(0),
    m1 => A_sel(1),
    m2 => A_sel(2),
    m3 => B_sel(0),

```

```

        m4 => B_sel(1),
        m5 => B_sel(2),
    Clk => Clk,
    Data_into_reg => Md_output,
    src_output_a => A_output ,
    src_output_b => B_output ,
    R0 => reg0_q,
    R1 => reg1_q,
    R2 => reg2_q,
    R3 => reg3_q,
    R4 => reg4_q,
    R5 => reg5_q,
    R6 => reg6_q,
    R7 => reg7_q
);
MB_select : Mux_2_1 port map(
    a => B_output,
    b => instruction_MB,
    sel => Mb_sel,
    g => Mb_output
);
MD_select : Mux_2_1 port map(
    a => functional_unit_output,
    b => data_in,
    sel => MD_sel,
    g => Md_output
);
Adrs_out <= A_output;
Data_out_bus_b <= B_output;
end Behavioral;

```

## Functional\_Unit.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Functional_Unit is
port(
    fsel : in std_logic_vector(4 downto 0);
    a : in std_logic_vector(15 downto 0);
    b : in std_logic_vector(15 downto 0);
    f : out std_logic_vector(15 downto 0);
    IL : in std_logic;
    IR : in std_logic;
    v : out std_logic;
    c : out std_logic;
    n : out std_logic;

```

```

        z : out std_logic
    );
end Functional_Unit;
architecture Behavioral of Functional_Unit is
-- signals
--input
signal A_input, B_input, B_shifter, ALU_output, Shifter_output, zero_detect_output : std_logic_vector(15 downto 0);
signal Shift_left_input, Shift_right_input, Shift_left_output, Shift_right_output, z_flag : std_logic;
--output
signal OUTPUT : std_logic_vector(15 downto 0);
-- add components
component ALU port(
    A, B : in std_logic_vector(15 downto 0);
    S1 : in std_logic;
    S2 : in std_logic;
    S3 : in std_logic;
    Cin : in std_logic;
    G : out std_logic_vector(15 downto 0);
    c : out std_logic
);
end component;
component Shifter port(
    IL : in std_logic;
    IR : in std_logic;
    s : in std_logic_vector(1 downto 0);
    b : in std_logic_vector (15 downto 0);
    O : out std_logic_vector(15 downto 0);
    SL0 : out std_logic;
    SR0 : out std_logic
);
end component;
component zeroDetect port(
    input : in std_logic_vector(15 downto 0);
    outputFlag : out std_logic;
    output : out std_logic_vector(15 downto 0)
);
end component;
component Mux_2_1 port(
    sel : in std_logic;
    a : in std_logic_vector(15 downto 0);
    b : in std_logic_vector(15 downto 0);
    g : out std_logic_vector(15 downto 0)
);
end component;

```

```

begin
Shift_left_input <= IR;
Shift_right_input <= IL;
ariLogUnit : ALU
port map(
    A => A,
    B => A,
    S3 => fsel(3),
    S2 => fsel(2),
    S1 => fsel(1),
    Cin => fsel(0),
    G => ALU_output,
    c => c
);
shift : Shifter
port map(
    IL => Shift_left_input,
    IR => Shift_right_input,
    S(1) => fsel(3),
    S(0) => fsel(2),
    b => b,
    O => Shifter_output,
    SL0 => Shift_left_output,
    SR0 => Shift_right_output
);
detect_Zero : zeroDetect
port map(
    input => ALU_output,
    outputFlag => z,
    output => zero_detect_output
);
MF_Select : Mux_2_1
port map(
    sel => fsel(4),
    a => zero_detect_output,
    b => Shifter_output,
    g => f
);

end Behavioral;

```

## Reg\_File.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Reg_File is
    Port (
        d0 : in  STD_LOGIC;
        d1 : in  STD_LOGIC;
        d2 : in  STD_LOGIC;
        m0 : in  STD_LOGIC;
        m1 : in  STD_LOGIC;
        m2 : in  STD_LOGIC;
        m3 : in  STD_LOGIC;
        m4 : in  STD_LOGIC;
        m5 : in  STD_LOGIC;
        data : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        dataS : in  STD_LOGIC;
        Clk : in  STD_LOGIC;
        Data_into_reg : in  STD_LOGIC_VECTOR(15 downto 0);

        src_output_a : out std_logic_vector(15 downto 0);
        src_output_b : out std_logic_vector(15 downto 0);

        R0 : out  STD_LOGIC_VECTOR(15 DOWNTO 0);
        R1 : out  STD_LOGIC_VECTOR(15 DOWNTO 0);
        R2 : out  STD_LOGIC_VECTOR(15 DOWNTO 0);
        R3 : out  STD_LOGIC_VECTOR(15 DOWNTO 0);
        R4 : out  STD_LOGIC_VECTOR(15 DOWNTO 0);
        R5 : out  STD_LOGIC_VECTOR(15 DOWNTO 0);
        R6 : out  STD_LOGIC_VECTOR(15 DOWNTO 0);
        R7 : out  STD_LOGIC_VECTOR(15 DOWNTO 0));
end Reg_File;

architecture Behavioral of Reg_File is
    -- Components
    -- reg16
    COMPONENT reg16
    PORT(
        D: IN STD_LOGIC_VECTOR(15 DOWNTO 0);
        load: IN STD_LOGIC;
```

```

        Clk: IN STD_LOGIC;
        Q: OUT STD_LOGIC_VECTOR(15 DOWNT0 0)
    );
END COMPONENT;
--3 to 8 decoder
COMPONENT Decoder38_16bit
PORT(
    S0: IN STD_LOGIC;
    S1: IN STD_LOGIC;
    S2: IN STD_LOGIC;
    dR0: OUT STD_LOGIC;
    dR1: OUT STD_LOGIC;
    dR2: OUT STD_LOGIC;
    dR3: OUT STD_LOGIC;
    dR4: OUT STD_LOGIC;
    dR5: OUT STD_LOGIC;
    dR6: OUT STD_LOGIC;
    dR7: OUT STD_LOGIC
);
END COMPONENT;
--8in 16 bit mux
COMPONENT Mux8in_16bit
PORT(
    S0: IN STD_LOGIC;
    S1: IN STD_LOGIC;
    S2: IN STD_LOGIC;
    R0: IN STD_LOGIC_VECTOR(15 downto 0);
    R1: IN STD_LOGIC_VECTOR(15 downto 0);
    R2: IN STD_LOGIC_VECTOR(15 downto 0);
    R3: IN STD_LOGIC_VECTOR(15 downto 0);
    R4: IN STD_LOGIC_VECTOR(15 downto 0);
    R5: IN STD_LOGIC_VECTOR(15 downto 0);
    R6: IN STD_LOGIC_VECTOR(15 downto 0);
    R7: IN STD_LOGIC_VECTOR(15 downto 0);
    OUTPUT: OUT STD_LOGIC_VECTOR(15 downto 0)
);
END COMPONENT;
--2 to 1 line multiplexer 16 bit
COMPONENT Small_Mux
PORT(
    In0: IN STD_LOGIC_VECTOR(15 downto 0);
    In1: IN STD_LOGIC_VECTOR(15 downto 0);
    S: IN STD_LOGIC;

```



```

        output: OUT STD_LOGIC_VECTOR(15 downto 0)
    );
END COMPONENT;

--signals
signal load_reg0, load_reg1, load_reg2, load_reg3, load_reg4, load_reg5,
load_reg6, load_reg7: STD_LOGIC;
signal reg0_q, reg1_q, reg2_q, reg3_q, reg4_q, reg5_q, reg6_q, reg7_q,
data_src_mux_out, src_regA , src_regB, Data_into_regput : STD_LOGIC_VECTOR(15 downto 0);
begin
--PORT MAPS
--register 0
reg00: reg16 PORT MAP (
    D => data_src_mux_out,
    load => load_reg0,
    Clk => Clk,
    Q => reg0_q
);
--register 1
reg01: reg16 PORT MAP (
    D => data_src_mux_out,
    load => load_reg1,
    Clk => Clk,
    Q => reg1_q
);
--register 2
reg02: reg16 PORT MAP (
    D => data_src_mux_out,
    load => load_reg2,
    Clk => Clk,
    Q => reg2_q
);
--register 3
reg03: reg16 PORT MAP (
    D => data_src_mux_out,
    load => load_reg3,
    Clk => Clk,
    Q => reg3_q
);
--register 4
reg04: reg16 PORT MAP (
    D => data_src_mux_out,
    load => load_reg4,
    Clk => Clk,
    Q => reg4_q
);

```

```

--register 5
reg05: reg16 PORT MAP (
    D => data_src_mux_out,
    load => load_reg5,
    Clk => Clk,
    Q => reg5_q
);

--register 6
reg06: reg16 PORT MAP (
    D => data_src_mux_out,
    load => load_reg6,
    Clk => Clk,
    Q => reg6_q
);

--register 7
reg07: reg16 PORT MAP (
    D => data_src_mux_out,
    load => load_reg7,
    Clk => Clk,
    Q => reg7_q
);

--Destination register decoder
-- will have to change this decoder..
des_decoder_3to8: Decoder38_16bit PORT MAP (
    S0 => d0,
    S1 => d1,
    S2 => d2,
    dR0 => load_reg0,
    dR1 => load_reg1,
    dR2 => load_reg2,
    dR3 => load_reg3,
    dR4 => load_reg4,
    dR5 => load_reg5,
    dR6 => load_reg6,
    dR7 => load_reg7
);

--2 to 1 Data Source Multiplexer
data_src_mux2: Small_Mux PORT MAP (
    In0 => data,
    In1 => Data_into_reg,
    S => dataS,

```

```

        output => data_src_mux_out
    );
    --8 to 1 source register multiplexer
    src_mux8: Mux8in_16bit PORT MAP (
        R0 => reg0_q,
        R1 => reg1_q,
        R2 => reg2_q,
        R3 => reg3_q,
        R4 => reg4_q,
        R5 => reg5_q,
        R6 => reg6_q,
        R7 => reg7_q,
        S0 => m0,
        S1 => m1,
        S2 => m2,
        OUTPUT => src_regA
    );
    src_mux8_B: Mux8in_16bit PORT MAP (
        R0 => reg0_q,
        R1 => reg1_q,
        R2 => reg2_q,
        R3 => reg3_q,
        R4 => reg4_q,
        R5 => reg5_q,
        R6 => reg6_q,
        R7 => reg7_q,
        S0 => m3,
        S1 => m4,
        S2 => m5,
        OUTPUT => src_regB
    );
    R0 <= reg0_q;
    R1 <= reg1_q;
    R2 <= reg2_q;
    R3 <= reg3_q;
    R4 <= reg4_q;
    R5 <= reg5_q;
    R6 <= reg6_q;
    R7 <= reg7_q;
    src_output_a <= src_regA;
    src_output_b <= src_regB;
    Data_into_regput <= Data_into_reg;
    Data_into_regput <= data_src_mux_out;
end Behavioral;

```

## Mux\_2\_1.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Mux_2_1 is
port(
    sel : in std_logic;
    a : in std_logic_vector(15 downto 0);
    b : in std_logic_vector(15 downto 0);
    g : out std_logic_vector(15 downto 0)
);
end Mux_2_1;
architecture Behavioral of Mux_2_1 is
begin
    g <= a after 1 ns when sel='0' else
    b after 1 ns when sel='1' else
    "0000000000000000" after 1 ns;

end Behavioral;
```

## ALU.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity ALU is
port(
    -- carry input??
    A, B : in std_logic_vector(15 downto 0);
    S1 : in std_logic;
    S2 : in std_logic;
    S3 : in std_logic;
    Cin : in std_logic; -- fS0
    G : out std_logic_vector(15 downto 0);
    c : out std_logic;
    v : out std_logic;
    n : out std_logic
);
end ALU;
```

architecture Behavioral of ALU is

-- signals input

signal arith\_out : std\_logic\_vector(15 downto 0);

signal logic\_out : std\_logic\_vector(15 downto 0);

-- signals output

signal output\_mux : std\_logic\_vector(15 downto 0);

signal output\_n\_flag : std\_logic;

component Arithmetic\_Circuit

port(

    A : in std\_logic\_vector(15 downto 0);

    B : in std\_logic\_vector(15 downto 0);

    S0 : in std\_logic;

    S1 : in std\_logic;

    Cin : in std\_logic;

    Cout : out std\_logic;

    G : out std\_logic\_vector(15 downto 0)

);

end component;

component logic\_circuit

port(

    A : in std\_logic\_vector(15 downto 0);

    B : in std\_logic\_vector(15 downto 0);

    S0 : in std\_logic;

    S1 : in std\_logic;

    G : out std\_logic\_vector(15 downto 0)

);

end component;

component Mux\_2\_1

port (

    sel : in std\_logic;

    A : in std\_logic\_vector(15 downto 0);

    B : in std\_logic\_vector(15 downto 0);

    G : out std\_logic\_vector(15 downto 0)

);

end component;

begin

ArithmeticCircuitry : Arithmetic\_Circuit

port map(

    A => A,

    B => B,

```

        S0 => S1,
        S1 => S2,
        Cin => Cin,
        Cout => c,
        G => arith_out
    );
LogicCircuit : logic_circuit
port map(
    A => A,
    B => B,
    S0 => S1,
    S1 => S2,
    G => logic_out
);
Mux2_1 : Mux_2_1
port map(
    sel => S3,
    A => arith_out,
    B => logic_out,
    G => output_mux
);
G <= output_mux;
output_n_flag <= '1' after 5 ns when (output_mux AND "1000000000000000") = "1000000000000000"
else '0' after 5 ns ;
n <= output_n_flag;

end Behavioral;

```

## Shifter.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Shifter is
port(
    IL : in std_logic;
    IR : in std_logic;
    s : in std_logic_vector(1 downto 0);
    b : in std_logic_vector (15 downto 0);
    O : out std_logic_vector(15 downto 0);

```

```
SLO : out std_logic;  
SRO : out std_logic  
);  
end Shifter;
```

architecture Behavioral of Shifter is

component shifter\_mux

port(  
    A : in std\_logic;  
    B : in std\_logic;  
    C : in std\_logic;  
    S : in std\_logic\_vector(1 downto 0);  
    H : out std\_logic  
);  
end component;

```
-- output signal  
signal S_0, S_1, S_2, S_3, S_4, S_5, S_6, S_7, S_8, S_9, S_10,  
S_11, S_12, S_13, S_14, S_15 : STD_LOGIC;  
begin
```

```
shifterMux00: shifter_mux Port map(  
    A => b(0),  
    B => b(1),  
    C => IL,  
    S => s,  
    H => S_0  
);
```

```
shifterMux01: shifter_mux Port map(  
    A => b(1),  
    B => b(2),  
    C => b(0),  
    S => s,  
    H => S_1  
);
```

```
shifterMux02: shifter_mux Port map(  
    A => b(2),  
    B => b(3),  
    C => b(1),  
    S => s,  
    H => S_2  
);
```

```
shifterMux03: shifter_mux Port map(
```

```
    A => b(3),
```

```
    B => b(4),
```

```
    C => b(2),
```

```
    S => s,
```

```
    H => S_3
```

```
);
```

```
shifterMux04: shifter_mux Port map(
```

```
    A => b(4),
```

```
    B => b(5),
```

```
    C => b(3),
```

```
    S => s,
```

```
    H => S_4
```

```
);
```

```
shifterMux05: shifter_mux Port map(
```

```
    A => b(5),
```

```
    B => b(6),
```

```
    C => b(4),
```

```
    S => s,
```

```
    H => S_5
```

```
);
```

```
shifterMux06: shifter_mux Port map(
```

```
    A => b(6),
```

```
    B => b(7),
```

```
    C => b(5),
```

```
    S => s,
```

```
    H => S_6
```

```
);
```

```
shifterMux07: shifter_mux Port map(
```

```
    A => b(7),
```

```
    B => b(8),
```

```
    C => b(6),
```

```
    S => s,
```

```
    H => S_7
```

```
);
```

```
shifterMux08: shifter_mux Port map(
```

```
    A => b(8),
```

```
    B => b(9),
```

```
    C => b(7),
```

```
    S => s,
```



```

        H => S_8
    );
    shifterMux09: shifter_mux Port map(
        A => b(9),
        B => b(10),
        C => b(8),
        S => s,
        H => S_9
    );
    shifterMux10: shifter_mux Port map(
        A => b(10),
        B => b(11),
        C => b(9),
        S => s,
        H => S_10
    );
    shifterMux11: shifter_mux Port map(
        A => b(11),
        B => b(12),
        C => b(10),
        S => s,
        H => S_11
    );
    shifterMux12: shifter_mux Port map(
        A => b(12),
        B => b(13),
        C => b(11),
        S => s,
        H => S_12
    );
    shifterMux13: shifter_mux Port map(
        A => b(13),
        B => b(14),
        C => b(12),
        S => s,
        H => S_13
    );
    shifterMux14: shifter_mux Port map(
        A => b(14),
        B => b(15),

```

```

        C => b(13),
        S => s,
        H => S_14
    );
shifterMux15: shifter_mux Port map(
    A => b(15),
    B => IR,
    C => b(14),
    S => s,
    H => S_15
);
SLO <= b(15);
SRO <= b(0);
O(0) <= s_0;
O(1) <= s_1;
O(2) <= s_2;
O(3) <= s_3;
O(4) <= s_4;
O(5) <= s_5;
O(6) <= s_6;
O(7) <= s_7;
O(8) <= s_8;
O(9) <= s_9;
O(10) <= s_10;
O(11) <= s_11;
O(12) <= s_12;
O(13) <= s_13;
O(14) <= s_14;
O(15) <= s_15;
end Behavioral;

```

## Detect\_zero.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity zeroDetect is
port(
    input : IN std_logic_vector(15 downto 0);
    outputFlag : OUT std_logic;
    output : out std_logic_vector(15 downto 0)
);
end zeroDetect;

```

```

architecture Behavioral of zeroDetect is
begin
    outputFlag <= '1' after 5 ns when (input OR "0000000000000000")=
        "0000000000000000" else
        '0' after 5 ns;
    output <= input;
end Behavioral;

```

## Arithmetic\_circuit.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Arithmetic_Circuit is
port(
    a : in std_logic_vector(15 downto 0);
    b : in std_logic_vector(15 downto 0);
    S0 : in std_logic;
    S1 : in std_logic;
    Cin : in std_logic;
    Cout : out std_logic;
    g : out std_logic_vector(15 downto 0)
);
end Arithmetic_Circuit;
architecture Behavioral of Arithmetic_Circuit is
-- signals
signal result_y : std_logic_vector(15 downto 0);
component B_Input_Logic
port(
    b : in std_logic_vector(15 downto 0);
    S0 : in std_logic;
    S1 : in std_logic;
    y : out std_logic_vector(15 downto 0)
);
end component;
component RippleAdder
port(
    B, A : in std_logic_vector(15 downto 0);
    C0 : in std_logic;
    S : out std_logic_vector(15 downto 0);
    C15 : out std_logic
);
end component;
begin
inputLogicB : B_Input_Logic
port map(
    b => b,

```

```

        S0 => S0,
        S1 => S1,
        y => result_y
    );
parallelAdd : RippleAdder port map(
    A => a,
    B => result_y,
    C0 => Cin,
    S => g,
    C15 => Cout
);
end Behavioral;

```

## Logic\_Circuit.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity logic_Circuit is
port(
    a : in std_logic_vector(15 downto 0);
    b : in std_logic_vector(15 downto 0);
    S1 : in std_logic;
    S0 : in std_logic;
    g : out std_logic_vector(15 downto 0)
);
end logic_Circuit;
--output signal
architecture Behavioral of logic_Circuit is
begin
    g <= (a AND b) after 1 ns when S1 ='0' and S0 ='0' else
    (a OR b) after 1 ns when S1 ='0' and S0 ='1' else
    (a XOR b) after 1 ns when S1 ='1' and S0 ='0' else
    (NOT a) after 1 ns when S1 ='1' and S0 ='1' else
    "0000000000000000" after 1 ns ;
end Behavioral;

```

## Shifter\_mux.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity shifter_mux is
port(
    A : in std_logic;
    B : in std_logic;
    C : in std_logic;
    S : in std_logic_vector(1 downto 0);

```

```

H : out std_logic
);
end shifter_mux;
architecture Behavioral of shifter_mux is
begin
H <= A after 5 ns when S="00" else
B after 5 ns when S= "01" else
C after 5 ns when S= "10" else
'0' after 5 ns;
end Behavioral;

```

## B\_input\_logic.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity B_Input_Logic is
port(
    b : in std_logic_vector(15 downto 0);
    S0 : in std_logic;
    S1 : in std_logic;
    y : out std_logic_vector(15 downto 0)
);
end B_Input_Logic;

architecture Behavioral of B_Input_Logic is
begin
    y <= "0000000000000000" after 1 ns when S1='0' and S0='0' else
    b after 1 ns when S1='0' and S0='1' else
    (Not b) after 1 ns when S1='1' and S0='0' else
    "1111111111111111" after 1 ns when S1='1' and S0='1' else
    "0000000000000000" after 1 ns;
end Behavioral;

```

## RippleAdder.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity RippleAdder is
port(
    B, A : in std_logic_vector(15 downto 0);
    C0 : in std_logic;
    S : out std_logic_vector(15 downto 0);
    C15 : out std_logic);
end RippleAdder;

architecture Behavioral of RippleAdder is
component Full_adder

```

```

port(
    x, y, z: in std_logic;
    s, c : out std_logic);
end component;
--Carry signals
signal C_1, C_2, C_3, C_4, C_5, C_6, C_7, C_8, C_9, C_10,
C_11, C_12, C_13, C_14, C_15: STD_LOGIC;
--Output bit signals
signal S_0, S_1, S_2, S_3, S_4, S_5, S_6, S_7, S_8, S_9, S_10,
S_11, S_12, S_13, S_14, S_15: STD_LOGIC;
signal C : std_logic_vector (16 downto 0);
--signal output : std_logic_vector(15 downto 0);
begin
    C(0) <= C0;
    Adder16:
    for i in 0 to 15 generate
        RAdd: Full_adder Port Map(
            x => A(i),
            y => B(i),
            z => C(i),
            s => S(i),
            c => C(i+1));
    end generate;
    C15 <= C(16);
end Behavioral;

```

## Test\_Benches.vhd

### DataPath\_test.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY Datapath_test IS
END Datapath_test;
ARCHITECTURE behavior OF Datapath_test IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT DataPath
    PORT(
        load_enable : in std_logic;
        instruction_MB : in std_logic_vector(15 downto 0);
        INL : in std_logic;
        INR : in std_logic;
        Data_in : in std_logic_vector(15 downto 0);
        Clk : in std_logic;

```

```

v : out std_logic;
c : out std_logic;
n : out std_logic;
z : out std_logic;
Adrs_out : out std_logic_vector(15 downto 0);
Data_out_bus_b : out std_logic_vector(15 downto 0);
Control_word : in std_logic_vector(16 downto 0)
    );
    END COMPONENT;
--Inputs

    signal load_enable : std_logic := '0';
    signal instruction_MB : std_logic_vector(15 downto 0) := (others => '0');
signal INL, INR : std_logic := '0';
    signal Data_in : std_logic_vector(15 downto 0) := (others => '0');
    signal Clk : std_logic := '0';
signal Control_word : std_logic_vector(16 downto 0) := (others => '0');


--Outputs
signal v : std_logic;
signal c : std_logic;
signal n : std_logic;
signal z : std_logic;
signal Adrs_out : std_logic_vector(15 downto 0);
signal Data_out_bus_b : std_logic_vector(15 downto 0);


-- Clock period definitions
constant Clk_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
    uut: DataPath PORT MAP (
        load_enable => load_enable,
        instruction_MB => instruction_MB,

INL => INL,
INR => INR,
        Data_in => Data_in,
        Clk => Clk,
        v => v,
        c => c,
        n => n,

```

```

    z => z,
    Adrs_out => Adrs_out,
    Data_out_bus_b => Data_out_bus_b,

Control_word => Control_word
);

-- Clock process definitions
Clk_process :process
begin
Clk <= '0';
wait for Clk_period/2;
Clk <= '1';
wait for Clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
-- first store values in registers
Control_word <= "00001000000000011"; -- write data in to register 0
Data_in <= "1010101010101010";
wait for 50 ns;
Control_word <= "11101000000000011"; -- write data in to register 8
Data_in <= "0101010101010101";
-- Can see the results working through the register file..
wait for 50 ns;
-- Control_word <= "11100000000000011"; -- write data in to register 1
wait for 50 ns;
Control_word <= "00100011100100001"; -- And instruction, dest 1, r0 0, r1 8, fs 01000, write
wait for 50 ns;
Control_word <= "00001000000000011"; -- write data in to register 0
Data_in <= "0000000011111111"; -- data in
wait for 50 ns;
Control_word <= "11001000000000011"; -- write data in to register 6
Data_in <= "1111111100000000"; -- data in
wait for 50 ns;
Control_word <= "10000011000001001"; -- Add instruction , dest R4, R0 0, R1 6, fs 00010, write
wait for 50 ns;
    wait for Clk_period*10;
    -- insert stimulus here

```




```
wait;
end process;
```


```
END;
```
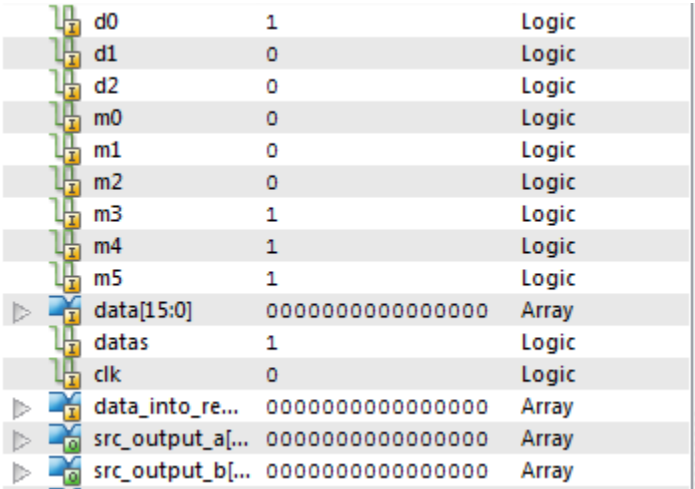
### DataPath\_test.vhd -WaveForm


Shows the values of the control word being added into selects for registers  
Control word = "00100011100100001"



Fs select being updated

 

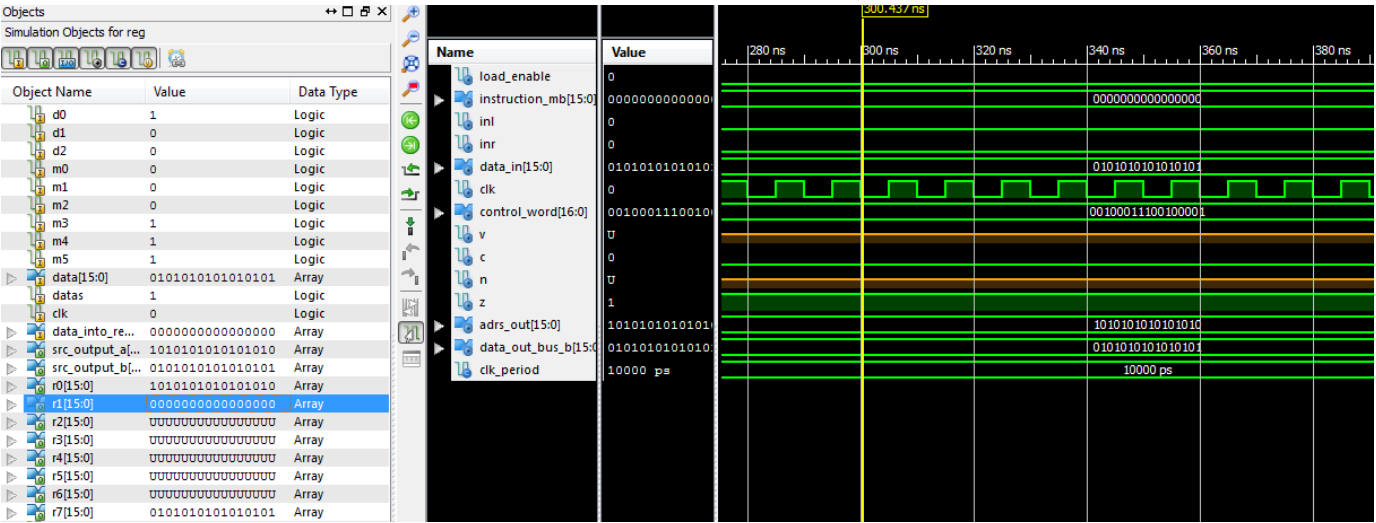After inserting the values into registers 0 and 7. The control word is updated to and registers 0 and 7 and store the result in R1. This is the case in the example below.



Close up of register results

data_into_re...	0000000000000000	Array
src_output_a[...	1010101010101010	Array
src_output_b[...	0101010101010101	Array
r0[15:0]	1010101010101010	Array
r1[15:0]	0000000000000000	Array
r2[15:0]	0000000000000000	Array
r3[15:0]	0000000000000000	Array
r4[15:0]	0000000000000000	Array
r5[15:0]	0000000000000000	Array
r6[15:0]	0000000000000000	Array
r7[15:0]	0101010101010101	Array

## Functional\_unit\_test.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
ENTITY Functional_unit_test IS
END Functional_unit_test;
ARCHITECTURE behavior OF Functional_unit_test IS
-- Component Declaration
    COMPONENT Functional_Unit
    PORT(
        fsel : in std_logic_vector(4 downto 0);
        a : in std_logic_vector(15 downto 0);
        b : in std_logic_vector(15 downto 0);
        f : out std_logic_vector(15 downto 0);
        IL : in std_logic;
        IR : in std_logic;
        v : out std_logic;
        c : out std_logic;
        n : out std_logic;
        z : out std_logic );
    END COMPONENT;
--output
    signal OUTPUT : std_logic_vector(15 downto 0) := (others => '0');
    signal v , c , n , z , IL, IR : std_logic := '0';
    signal fsel : std_logic_vector(4 downto 0) := (others => '0');
    signal a, b, f : std_logic_vector(15 downto 0) := (others => '0');
    BEGIN
-- Component Instantiation
        uut: Functional_Unit PORT MAP(
            fsel => fsel,
            a => a,
            b => b,
            f => f,
            IL => IL,
            IR => IR,

```

```

        v => v,
        c => c,
        n => n,
        z => z
    );
-- Test Bench Statements
tb : PROCESS
BEGIN

    wait for 20 ns; -- wait until global set/reset completes
    IL <= '0';
    IR <= '0';
    a <= "0000111100001111";
    b <= "0000101010101010";
        wait for 20 ns; -- F = A;
        fsel <= "00000";
        wait for 20 ns; -- F = A+1;
        fsel <= "00001";
        wait for 20 ns; -- F = A + B;
        fsel <= "00010";
        wait for 20 ns; -- F = A+ B +1;
        fsel <= "00011";
        wait for 20 ns; -- F = A+ NOTB
        fsel <= "00100";
        wait for 20 ns; -- F = A+ notB +1 -- subtract
        fsel <= "00101";
        wait for 20 ns; -- F = A -1
        fsel <= "00110";
        wait for 20 ns; -- F = A
        fsel <= "00111";
        wait for 20 ns; -- F = A AND B
        fsel <= "01000";
        wait for 20 ns; -- F = A OR B
        fsel <= "01010";
        wait for 20 ns; -- F = A XOR B
        fsel <= "01100";
        wait for 20 ns; -- F = NOT A
        fsel <= "01110";
        wait for 20 ns; -- F = B
        fsel <= "10000";
        wait for 20 ns; -- F = sr B
        fsel <= "10100";
        wait for 20 ns; -- F = sl B
        fsel <= "11000";

```

```

        wait for 20 ns; -- F = sr B
        wait; -- will wait forever
    END PROCESS tb;
-- End Test Bench
END;

```

## Functional\_unit - Waveforms



## Reg\_file\_test.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

ENTITY Reg_File_Test IS
END Reg_File_Test;
ARCHITECTURE behavior OF Reg_File_Test IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT Reg_File
    Port (
    d0 : in STD_LOGIC;
        d1 : in STD_LOGIC;
        d2 : in STD_LOGIC;
        m0 : in STD_LOGIC;
        m1 : in STD_LOGIC;
        m2 : in STD_LOGIC;
    m3 : in STD_LOGIC;
    m4 : in STD_LOGIC;
    m5 : in STD_LOGIC;
        data : in STD_LOGIC_VECTOR(15 DOWNTO 0);

```

```

    dataS : in STD_LOGIC;
    Clk : in STD_LOGIC;
Data_into_reg : in STD_LOGIC_VECTOR(15 downto 0);
src_output_a : out std_logic_vector(15 downto 0);
src_output_b : out std_logic_vector(15 downto 0);


    R0 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R1 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R2 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R3 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R4 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R5 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R6 : out STD_LOGIC_VECTOR(15 DOWNTO 0);
    R7 : out STD_LOGIC_VECTOR(15 DOWNTO 0));
END COMPONENT;


--Inputs
signal d0 : std_logic := '0';
signal d1 : std_logic := '0';
signal d2 : std_logic := '0';
signal m0 : std_logic := '0';
signal m1 : std_logic := '0';
signal m2 : std_logic := '0';
signal m3 : std_logic := '0';
signal m4 : std_logic := '0';
signal m5 : std_logic := '0';
signal Data_into_reg : std_logic_vector(15 downto 0) := (others => '0');
signal Clk : std_logic := '0';
signal dataS : std_logic := '0';
signal data : std_logic_vector(15 downto 0) := (others => '0');
--Outputs
signal src_output_a : std_logic_vector (15 downto 0);
signal src_output_b : std_logic_vector (15 downto 0);
signal R0 : std_logic_vector(15 downto 0);
signal R1 : std_logic_vector(15 downto 0);
signal R2 : std_logic_vector(15 downto 0);
signal R3 : std_logic_vector(15 downto 0);
signal R4 : std_logic_vector(15 downto 0);
signal R5 : std_logic_vector(15 downto 0);
signal R6 : std_logic_vector(15 downto 0);
signal R7 : std_logic_vector(15 downto 0);


-- Clock period definitions
constant CLK_period : time := 10 ns;

```

BEGIN

-- Instantiate the Unit Under Test (UUT)

   uut: Reg\_File PORT MAP (

    d0 => d0,

    d1 => d1,

    d2 => d2,

    m0 => m0,

    m1 => m1,

    m2 => m2,

  m3 => m3,

  m4 => m4,

  m5 => m5,

  Data\_into\_reg => Data\_into\_reg,

  dataS => dataS,

  src\_output\_a => src\_output\_a,

  src\_output\_b => src\_output\_b,

  data => data,

    CLK => CLK,

    R0 => R0,

    R1 => R1,

    R2 => R2,

    R3 => R3,

    R4 => R4,

    R5 => R5,

    R6 => R6,

    R7 => R7

  );

-- Clock process definitions

  CLK\_process :process

  begin

  CLK <= '0';

  wait for CLK\_period/2;

  CLK <= '1';

  wait for CLK\_period/2;

  end process;

-- Stimulus process

  stim\_proc: process

  begin

    -- hold reset state for 100 ns.

  wait for CLK\_period;

```
-- insert stimulus here
--Allow writing to registers
dataS <= '0';
--Select R0
d0 <= '0';
d1 <= '0';
d2 <= '0';
data <= "0000000000000001";
wait for CLK_period*2;
--Select R1
d0 <= '1';
d1 <= '0';
d2 <= '0';
data <= "0000000000000010";
wait for CLK_period*2;
--Select R2
d0 <= '0';
d1 <= '1';
d2 <= '0';
data <= "0000000000000100";
wait for CLK_period*2;
--Select R3
d0 <= '1';
d1 <= '1';
d2 <= '0';
data <= "0000000000001000";
wait for CLK_period*2;
--Select R4
d0 <= '0';
d1 <= '0';
d2 <= '1';
data <= "000000000010000";
wait for CLK_period*2;
--Select R5
d0 <= '1';
d1 <= '0';
d2 <= '1';
data <= "000000000100000";
wait for CLK_period*2;
--Select R6
d0 <= '0';
d1 <= '1';
d2 <= '1';
data <= "000000000100000";
wait for CLK_period*2;
```

```
--Select R7
d0 <= '1';
d1 <= '1';
d2 <= '1';
data <= "0101010101010101";
wait for CLK_period*2;
--Now load into different registers
dataS <= '1';
--Move R7 to other registers
--Select R7 with mux
m0 <= '1';
m1 <= '1';
m2 <= '1';
wait for CLK_period*2;
--Select R0 with decoder
d0 <= '0';
d1 <= '0';
d2 <= '0';
wait for CLK_period*2;
--Select R1 with decoder
d0 <= '1';
d1 <= '0';
d2 <= '0';
wait for CLK_period*2;
--Select R2 with decoder
d0 <= '0';
d1 <= '1';
d2 <= '0';
wait for CLK_period*2;
--Select R3 with decoder
d0 <= '1';
d1 <= '1';
d2 <= '0';
wait for CLK_period*2;
--Select R4 with decoder
d0 <= '0';
d1 <= '0';
d2 <= '1';
wait for CLK_period*2;
--Select R5 with decoder
d0 <= '1';
d1 <= '0';
d2 <= '1';
wait for CLK_period*2;
--Select R6 with decoder
```




```

d0 <= '0';
d1 <= '1';
d2 <= '1';
wait for CLK_period*2;
--Select R7 with decoder
d0 <= '1';
d1 <= '1';
d2 <= '1';
wait for CLK_period*2;
    wait;
end process;
END;

```

## Reg\_file\_test – Waveforms

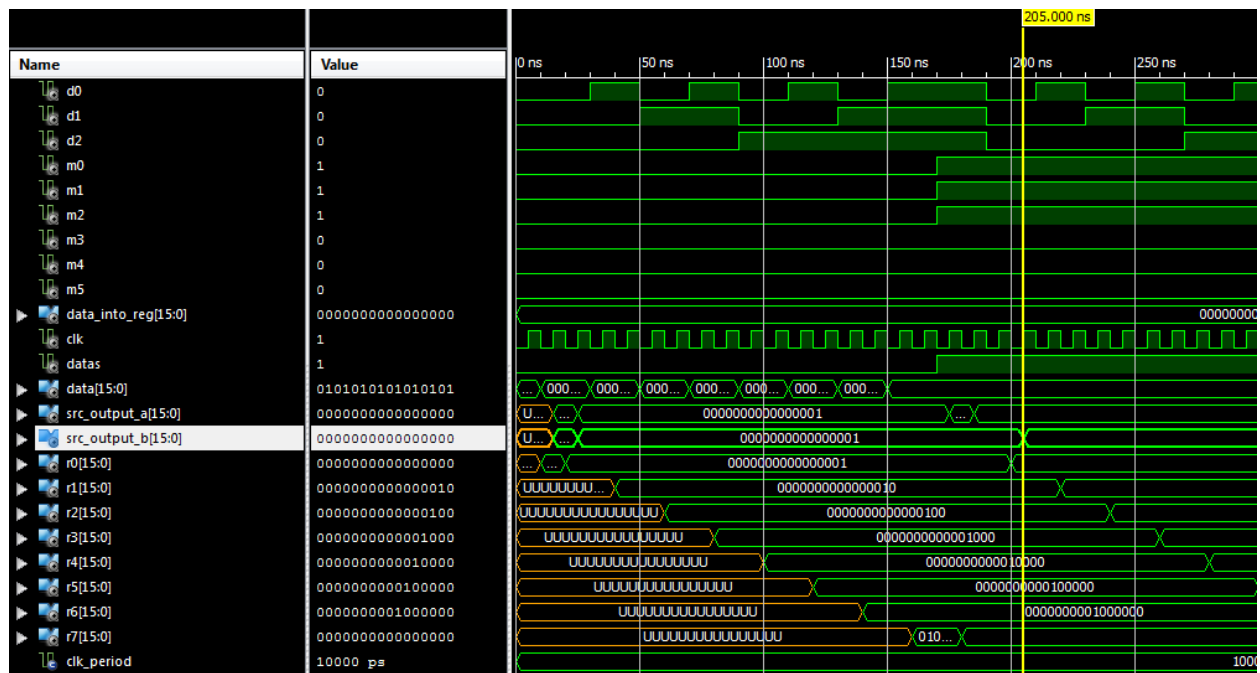

## ALU\_test.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY ALU_test IS
END ALU_test;

ARCHITECTURE behavior OF ALU_test IS

```

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT ALU

PORT(

A, B : in std\_logic\_vector(15 downto 0);

S1 : in std\_logic;

S2 : in std\_logic;

S3 : in std\_logic;

Cin : in std\_logic; -- fS0

G : out std\_logic\_vector(15 downto 0);

c : out std\_logic;

v : out std\_logic;

n : out std\_logic

);

END COMPONENT;

--Inputs

signal S1 : std\_logic := '0';

signal S2 : std\_logic := '0';

signal S3 : std\_logic := '0';

signal Cin : std\_logic := '0'; --fS1

signal A : std\_logic\_vector(15 downto 0) := (others => '0');

signal B : std\_logic\_vector(15 downto 0) := (others => '0');

--Outputs

signal G : std\_logic\_vector(15 downto 0) := (others => '0');

signal cOut : std\_logic := '0';

signal v : std\_logic := '0';

signal c : std\_logic := '0';

signal n : std\_logic := '0';

signal z : std\_logic := '0';

-- No clocks detected in port list. Replace <clock> below with

-- appropriate port name

BEGIN

-- Instantiate the Unit Under Test (UUT)

uut: ALU PORT MAP (

```

        S1 => S1,
S2 => S2,
S3 => S3,
        A => A,
        B => B,
        G => G,
Cin => Cin,
        v => v,
        c => c,
        n => n
    );

```

```

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 20 ns;
A <= "0000000000110000";
B <= "0000000011000000";
-- g == A
Cin <= '0';
S3 <= '0';
S2 <= '0';
S1 <= '0';
wait for 100 ns; -- g == A+1
Cin <= '1';
wait for 100 ns; -- g == A + B
Cin <= '0';
S3 <= '0';
S2 <= '0';
S1 <= '1';
wait for 100 ns; -- g = A + B + 1
Cin <= '1';
wait for 100 ns; -- g = A + B .. not sure
Cin <= '0';
S3 <= '0';
S2 <= '1';
S1 <= '0';
wait for 100 ns; -- g = A + B + 1
Cin <= '1';

```

```

wait for 30 ns; -- g = A - 1
Cin <= '0';
S3 <= '0';
S2 <= '1';
S1 <= '1';
wait for 30 ns; -- g = A
Cin <= '1';
wait for 30 ns; -- g = A and B
S3 <= '1';
S2 <= '0';
S1 <= '0';
wait for 30 ns; -- g = A OR B
-- dont need to continuously change s2 but Just to make it clear
S3 <= '1';
S2 <= '0';
S1 <= '1';
wait for 30 ns; -- g =A XOR B
S3 <= '1';
S2 <= '1';
S1 <= '0';
wait for 30 ns; -- g = NOT A
S3 <= '1';
S2 <= '1';
S1 <= '1';
wait for 30 ns; --
    -- insert stimulus here
    wait;
end process;
END;

```

## ALU\_test - Waveforms



## Shifter\_test.vhd

-- TestBench Template

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
```

-- TestBench Template

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
```

ENTITY Shifter\_test IS

END Shifter\_test;

ARCHITECTURE behavior OF Shifter\_test IS

-- Component Declaration for the Unit Under Test (UUT)

```
COMPONENT Shifter
PORT(
IL : in std_logic;
IR : in std_logic;
s : in std_logic_vector(1 downto 0);
b : in std_logic_vector (15 downto 0);
```

```

O : out std_logic_vector(15 downto 0);
SLO : out std_logic;
SRO : out std_logic
    );
    END COMPONENT;

--Inputs
signal b : std_logic_vector(15 downto 0) := (others => '0');
signal s : std_logic_vector(1 downto 0) := (others => '0');
signal IR : std_logic := '0';
signal IL : std_logic := '0';
--outputs
signal O : std_logic_vector(15 downto 0) := (others => '0');
signal SLO : std_logic := '0';
signal SRO : std_logic := '0';

--Outputs
signal output : std_logic_vector(15 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

BEGIN

-- Instantiate the Unit Under Test (UUT)
    uut: Shifter PORT MAP (
        IL => IL,
        IR => IR,
        s => s,
        b => b,
        O => O,
        SLO => SLO,
        SRO => SRO

    );
    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 10 ns;

```

```
-- insert stimulus here
b <= "0000101010101010" ;

--Set for In0
s <= "00";

wait for 20 ns;

--Set for In1
s <= "01";

wait for 10 ns;

s <= "10";


wait for 10 ns;

    wait;

end process;

END;
```

## Shifter\_test - Waveforms

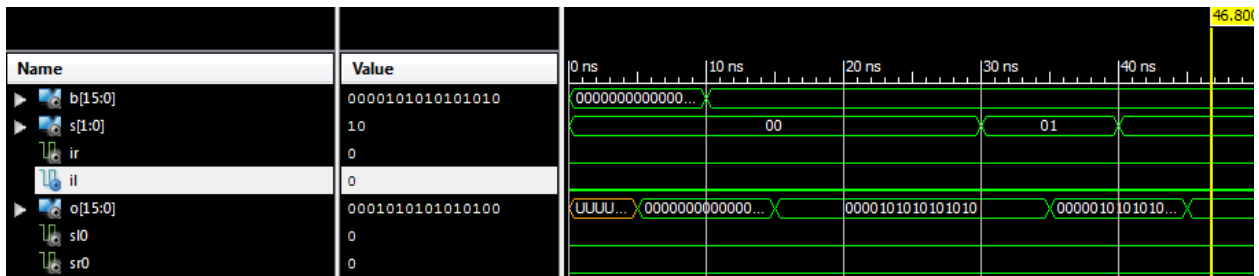

## Arithmetic\_circuit\_test.vhd

## -- TestBench Template

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.numeric_std.ALL;

ENTITY Arithmetic_circuit_test IS

END Arithmetic_circuit_test;

ARCHITECTURE behavior OF Arithmetic_circuit_test IS

-- Component Declaration

    COMPONENT Arithmetic_Circuit

    PORT(

        a : in std_logic_vector(15 downto 0);

        b : in std_logic_vector(15 downto 0);

        S0 : in std_logic;

        S1 : in std_logic;

        Cin : in std_logic;

```

```

Cout : out std_logic;
g : out std_logic_vector(15 downto 0)
);
    END COMPONENT;
-- inputs
    SIGNAL S0 : std_logic := '0';
signal S1 : std_logic := '0';
signal Cin : std_logic := '0';

    SIGNAL a : std_logic_vector(15 downto 0) := (others => '0');
    signal b : std_logic_vector(15 downto 0) := (others => '0');
signal Cout : std_logic := '0';
-- outputs
signal g : std_logic_vector(15 downto 0) := (others => '0');
BEGIN

-- Component Instantiation
    uut: Arithmetic_Circuit PORT MAP(
        a => a,
        b => b,
        S0 => S0,
        S1 => S1,
        Cin => Cin,
        Cout => Cout,
        g => g
    );


-- Test Bench Statements
    tb : PROCESS
    BEGIN
        wait for 20 ns; -- wait until global set/reset completes
A <= "0000000000110000";
B <= "0000000011000000";
wait for 20 ns;
S1 <= '0';
S0 <= '0';
Cin <= '0';
wait for 20 ns;
Cin <= '1';
wait for 20 ns;

```



```
S1 <= '0';
S0 <= '1';
Cin <= '0';
wait for 20 ns;
Cin <= '1';
wait for 20 ns;
S1 <= '1';
S0 <= '0';
Cin <= '0';
wait for 20 ns;
Cin <= '1';
wait for 20 ns;
S1 <= '1';
S0 <= '1';
Cin <= '0';
wait for 20 ns;
Cin <= '1';
wait for 20 ns;
    -- Add user defined stimulus here
```
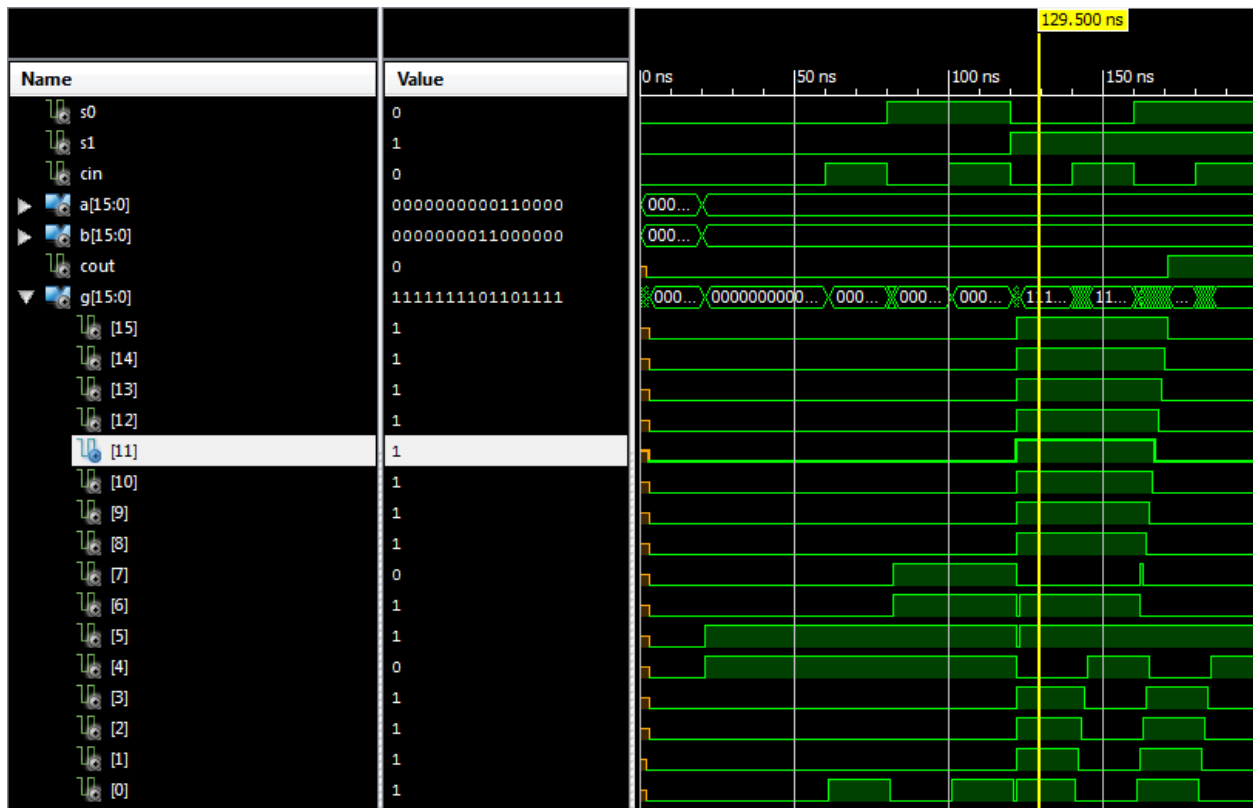
```
    wait; -- will wait forever
END PROCESS tb;
-- End Test Bench
END;
```



## Logic\_circuit\_test.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY logic_circuit_test IS
END logic_circuit_test;
ARCHITECTURE behavior OF logic_circuit_test IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT logic_Circuit
    PORT(
        a : IN std_logic_vector(15 downto 0);
        b : IN std_logic_vector(15 downto 0);
        S0 : IN std_logic;
        S1 : IN std_logic;
        g : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal a : std_logic_vector(15 downto 0) := (others => '0');
    signal b : std_logic_vector(15 downto 0) := (others => '0');
    signal S0 : std_logic := '0';

```

```


signal S1 : std_logic := '0';

--Outputs
signal g : std_logic_vector(15 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name
BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: logic_Circuit PORT MAP (
    a => a,
    b => b,
    S0 => S0,
    S1 => S1,
    g => g
  );
-- Stimulus process
stim_proc: process
begin
  -- hold reset state for 100 ns.
  wait for 20 ns;
  a <= "0000000000000001";
  b <= "0000000000001111";
  wait for 10 ns;
  S0 <= '0';
  S1 <= '0';
  wait for 10 ns;
  S0 <= '1';
  S1 <= '0';
  wait for 10 ns;
  S0 <= '0';
  S1 <= '1';
  wait for 10 ns;
  S0 <= '1';
  S1 <= '1';
  -- insert stimulus here
  wait;
end process;

END;

```

 

## RippleAdder\_test.vhd

```
-- TestBench Template
```

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.ALL;
```

```
USE ieee.numeric_std.ALL;
```

```
ENTITY RippleAdder_test IS
```

```
END RippleAdder_test;
```

```
ARCHITECTURE behavior OF RippleAdder_test IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT RippleAdder
```

```
PORT(
```

```
    B, A : in std_logic_vector(15 downto 0);
```

```
C0 : in std_logic; -- input
```

```
S : out std_logic_vector(15 downto 0);
```

```
C15 : out std_logic -- output
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal B : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal A : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal C0 : std_logic := '0';
```

```
--Outputs
```

```
signal s : std_logic_vector(15 downto 0);
```

```
signal C15 : std_logic := '0';
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
BEGIN
```


```
-- Instantiate the Unit Under Test (UUT)
```

```
    uut: RippleAdder PORT MAP (
```

```

    A => A,
    B => B,
    S => S,
    C0 => C0,
C15 => C15
);
-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 20 ns;
    -- insert stimulus here
A <= "0000000100010001";
B <= "0000000100010001";
--Set for a
C0 <= '0';
wait for 20 ns;
--Set for b
wait for 20 ns;
B <= x"FFFF";
wait for 20 ns;
A <= x"0001";
wait for 20 ns;
A<= x"8000";
B<= x"8000";
wait for 20 ns;
    wait;
    end process;
END;

```

 

## BInput\_logic\_test.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY B_input_logic_test IS

```

```
END B_input_logic_test;
```

```
ARCHITECTURE behavior OF B_input_logic_test IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT B_Input_Logic
```

```
PORT(
```

```
    b : IN std_logic_vector(15 downto 0);
```

```
    S0 : IN std_logic;
```

```
    S1 : IN std_logic;
```

```
    y : OUT std_logic_vector(15 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal b : std_logic_vector(15 downto 0) := (others => '0');
```

```
signal S0 : std_logic := '0';
```

```
signal S1 : std_logic := '0';
```

```
--Outputs
```

```
signal y : std_logic_vector(15 downto 0) := (others => '0');
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
    uut: B_Input_Logic PORT MAP (
```

```
        b => b,
```

```
        S0 => S0,
```

```
        S1 => S1,
```

```
        y => y
```

```
    );
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
begin
```

```
    -- hold reset state for 100 ns.
```

```
    wait for 20 ns;
```

```
b <= "0000000000000000";
```

```
wait for 5 ns;
```

```
S0 <= '0';
```

```
S1 <= '0';
```

```
wait for 10 ns;
```

```
S0 <= '0';
```


```
S1 <= '1';
```

```
wait for 10 ns;
```

```

S0 <= '1';
S1 <= '0';
wait for 10 ns;
S0 <= '1';
S1 <= '1';
wait for 10 ns;
    -- insert stimulus here
    wait;
end process;
END;

```

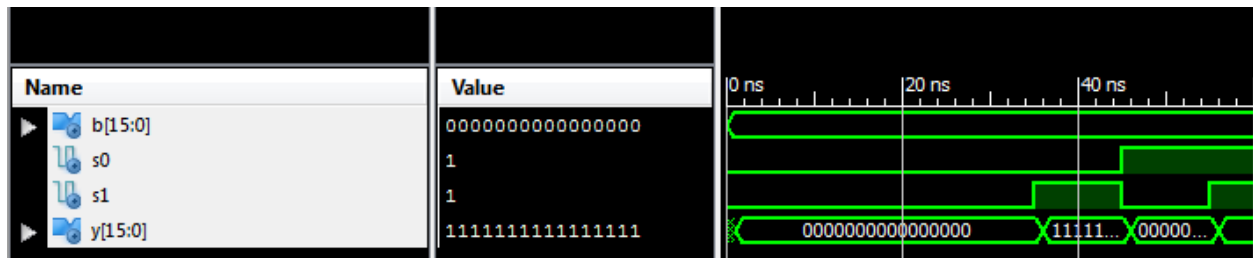

## Detect\_zero\_test.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY zeroDetect_test IS
END zeroDetect_test;
ARCHITECTURE behavior OF zeroDetect_test IS
    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT zeroDetect
    PORT(
        input : IN  std_logic_vector(15 downto 0);
        outputFlag : OUT std_logic;
        output : out std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal input : std_logic_vector(15 downto 0) := (others => '0');
    --Outputs
    signal output : std_logic_vector(15 downto 0) := (others => '0');
    signal outputFlag : std_logic;
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name
BEGIN

    -- Instantiate the Unit Under Test (UUT)

```


```

    uut: zeroDetect PORT MAP (
        input => input,
        outputFlag => outputFlag,
        output => output
    );
    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 20 ns;
        input <= "1111111111111111";
        wait for 10 ns;

        input <= "0000000000000000";
        wait for 10 ns;
        -- insert stimulus here

        wait;
    end process;
END;

```

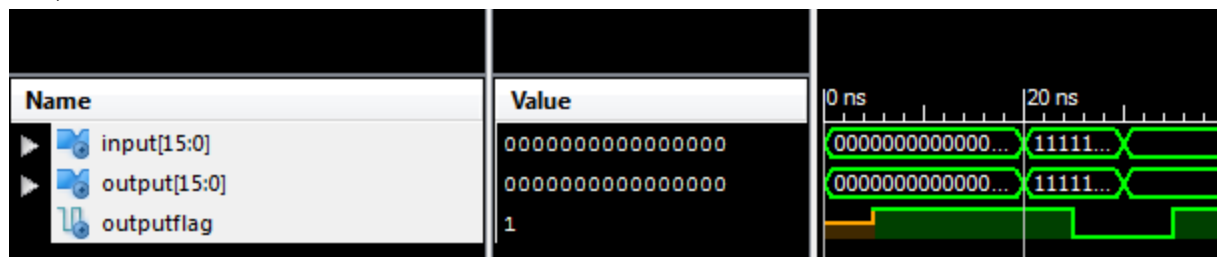

## Mux\_2\_1\_test.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY Mux2_1_test IS
END Mux2_1_test;
ARCHITECTURE behavior OF Mux2_1_test IS
    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Mux_2_1
    PORT(
        sel : IN std_logic;
        a : IN std_logic_vector(15 downto 0);
        b : IN std_logic_vector(15 downto 0);
        g : OUT std_logic_vector(15 downto 0)
    );
END COMPONENT;

```




```

--Inputs
signal sel : std_logic := '0';
signal a : std_logic_vector(15 downto 0) := (others => '0');
signal b : std_logic_vector(15 downto 0) := (others => '0');
--Outputs
signal g : std_logic_vector(15 downto 0);
-- No clocks detected in port list. Replace <clock> below with
BEGIN

-- Instantiate the Unit Under Test (UUT)
 uut: Mux_2_1 PORT MAP (
     sel => sel,
     a => a,
     b => b,
     g => g
 );
-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 20 ns;
a <= "0000000000000000";
b <= "0000000000000001";
wait for 10 ns;
sel <= '0';
wait for 10 ns;
sel <= '1';
    -- insert stimulus here
    wait;
end process;
END;

```

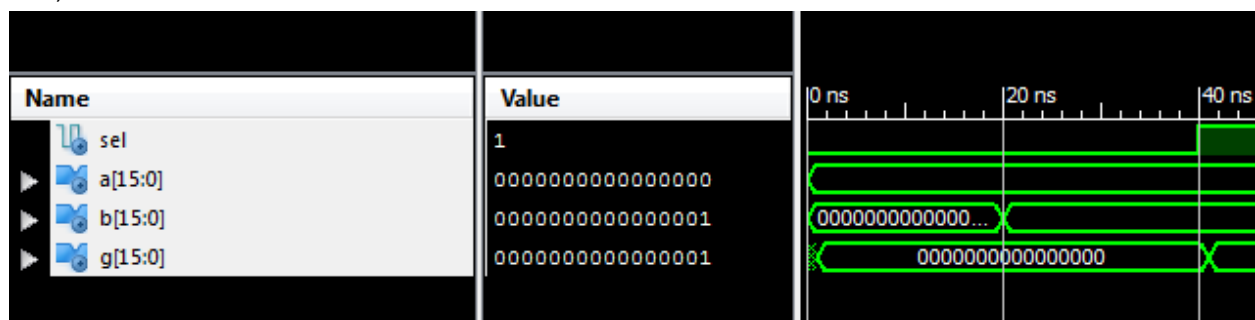

## Shifter\_mux\_test.vhd

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```
ENTITY ShifterMux_test IS
END ShifterMux_test;
```

```
ARCHITECTURE behavior OF ShifterMux_test IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT shifter_mux
```

```
PORT(
```

```
    A : IN std_logic;
```

```
    B : IN std_logic;
```

```
    C : IN std_logic;
```

```
    S : IN std_logic_vector(1 downto 0);
```

```
    H : OUT std_logic
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic := '0';
```

```
signal B : std_logic := '0';
```

```
signal C : std_logic := '0';
```

```
signal S : std_logic_vector(1 downto 0) := (others => '0');
```

```
--Outputs
```

```
signal H : std_logic;
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: shifter_mux PORT MAP (
```

```
    A => A,
```

```
    B => B,
```

```
    C => C,
```

```
    S => S,
```

```
    H => H
```

```
);
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
begin
```

```
    -- hold reset state for 100 ns.
```

```
    wait for 20 ns;
```

```
S <= "00";
```

```
wait for 10 ns;
```

```

A <= '1';
wait for 10 ns;
S<= "01";
A <= '0';
wait for 10 ns;
B <= '1';
wait for 10 ns;
S<= "10";
wait for 10 ns;
C <= '1';
B <= '0';
wait for 20 ns;
    -- insert stimulus here
    wait;
end process;

END;

```

